

## LAB # 02

Develop, implement & simulate Full Adder & Half Adder through Schematic & Gate Level Modeling

Objective: Develop, implement & simulate Half Adder & Full Adder through Schematic & Gate Level Modeling.

Task 1: Develop, implement & simulate Half Adder through Schematic & Gate Level Modeling

```

`timescale 1ns / 1ps
module HalfAdderTf;
  // Inputs
  reg a;
  reg b;
  // Outputs
  wire sum;
  wire carry;
  // Instantiate the Unit Under Test (UUT)
  HalfAdderModule uut (
    .a(a),
    .b(b),
    .sum(sum),
    .carry(carry)
  );
  initial begin
    // Initialize Inputs
    a = 0; b = 0;
    #100;
    a = 0; b = 0;
    #100;
    a = 0; b = 1;
    #100;
    a = 1; b = 0;
    #100;
    a = 1; b = 1;
    #100;
    // Wait 100 ns for global reset to finish
    // Add stimulus here
  end
endmodule



```

```

`timescale 1ns / 1ps
module HalfAdderModule(
  input a,
  input b,
  output sum,
  output carry
);

xor(sum,a,b);
and(carry,a,b);
endmodule

```

 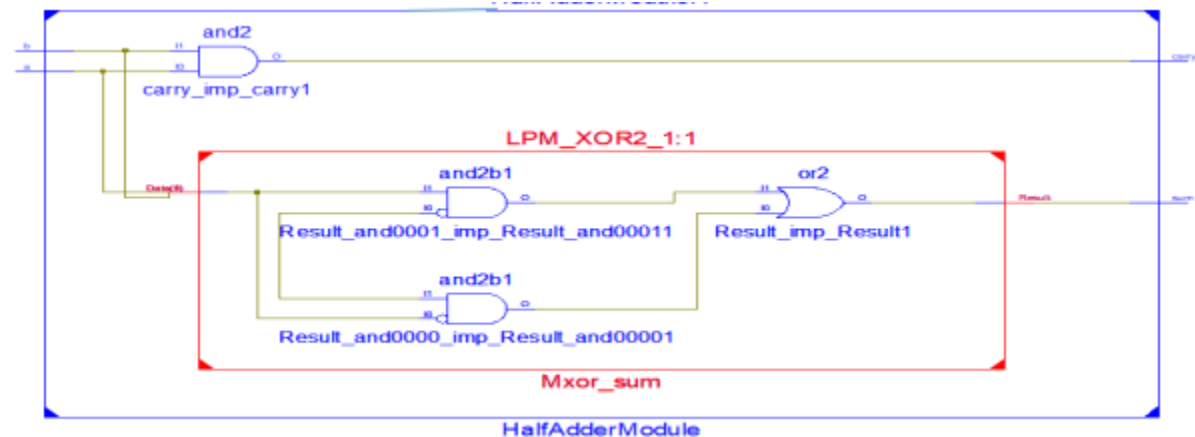

## Task 2: Develop, implement &amp; simulate Full Adder using schematic &amp; Gate Level Modeling

```

`timescale 1ns / 1ps
module FullAdderModule(
    input a,
    input b,
    input cin,
    inout s1,
    inout c1,
    inout c2,
    output sum,
    output cout
);
xor(s1,a,b);
xor(sum,s1,cin);
and(c1,cin,s1);
and(c2,a,b);
or(cout,c1,c2);_
endmodule

`timescale 1ns / 1ps
module FullAdderTf;
// Inputs
reg a;
reg b;
reg cin;
// Outputs
wire sum;
wire cout;
// Bidirs
wire s1;
wire c1;
wire c2;
// Instantiate the Unit Under Test (UUT)
FullAdderModule uut (
    .a(a),
    .b(b),
    .cin(cin),
    .s1(s1),
    .c1(c1),
    .c2(c2),
    .sum(sum),
    .cout(cout)
);
initial begin
    // Initialize Inputs
    a = 0;
    b = 0;
    cin = 0;
    // Wait 100 ns for global reset to finish
    #100;
    a=0; b=0; #100;
end

```

