

**LAB # 06****OBJECTIVE** : Develop, implement & simulate Dadda wallance Tree.**Lab Task 1**

Implement &amp; simulate 4X4 Dadda Wallance Tree.

**Verilog Module code:**

```

23 module WallaceMul(
24     input [3:0] a,
25     input [3:0] b,
26     output [7:0] product
27 );
28
29     wire s0,s1,s2,s3,s4,s5,s6,s7,s8,s9,s10,s11,c0,c1,
30     c2,c3,c4,c5,c6,c7,c8,c9,c10,c11;
31     // sums & carries generated by FA
32
33     reg p[3:0][3:0]; // double array for partial products
34     integer i,j;
35
36
37     always@(a or b)
38     begin
39         for(i=0;i<=3;i=i+1) // nested for loops.
40             for(j=0;j<=3;j=j+1)
41                 p[i][j]<= a[j] & b[i]; // to generate partial products.
42
43     end
44
45     Halfadder HA0(p[1][0],p[0][1],s0,c0);
46     Fulladder FA0(p[0][2],p[1][1],p[2][0],s1,c1);
47     Fulladder FA1(p[0][3],p[1][2],p[2][1],s2,c2);
48     Halfadder HA1(p[1][3],p[2][2],s3,c3);
49
50     Halfadder HA2(s1,c0,s4,c4);
51     Fulladder FA2(p[3][0],s2,c1,s5,c5);
52     Fulladder FA3(p[3][1],s3,c2,s6,c6);
53     Fulladder FA4(p[3][2],p[2][3],c3,s7,c7);
54
55     Halfadder HA3(s5,c4,s8,c8);
56     Fulladder FA5(s6,c5,c8,s9,c9);
57     Fulladder FA6(s7,c6,c9,s10,c10);
58     Fulladder FA7(p[3][3],c7,c10,s11,c11);
59
60
61     assign product[0]=p[0][0];
62     assign product[1]=s0;
63     assign product[2]=s4;
64     assign product[3]=s8;
65     assign product[4]=s9;
66     assign product[5]=s10;
67     assign product[6]=s11;
68     assign product[7]=c11;
69
70
71 imodule
72


```

**Verilog test fixture code:**

```

26 module WallaceMulTF;
27
28     // Inputs
29     reg [3:0] a;
30     reg [3:0] b;
31
32     // Outputs
33     wire [7:0] product;
34     // Instantiate the Unit Under Test (UUT)
35     WallaceMul uut (
36         .a(a),
37         .b(b),
38         .product(product)
39     );
40     initial begin
41         // Initialize Inputs
42         a = 0;
43         b = 0;
44         // Wait 100 ns for global reset to finish
45         #100;
46         // Add stimulus here
47         a=4'b1000;
48         b=4'b1000;
49     end
50 endmodule

```

 **WAVEFORM:****Lab Task 2**

To Develop, Implement and Simulate 6x6 Dadda Wallace Tree.

**Verilog Module code:**

```

23 module WallaceMul (
24     input [7:0] a,
25     input [7:0] b,
26     output [12:0] product
27 );
28
29     wire s1,s2,s3,s4,s5,s6,s7,s8,s9,s10,s11,s12,s13,s14,s15,
30     s16,s17,s18,s19,s20,s21,s22,s23,s24,s25,s26,s27,s28,s29,
31     s30,s31,s32,s33,s34,c1,c2,c3,c4,c5,c6,c7,c8,c9,c10,c11,
32     c12,c13,c14,c15,c16,c17,c18,c19,c20,c21,c22,c23,c24,c25,
33     c26,c27,c28,c29,c30,c31,c32,c33,c34;
34     // sums & carries generated by FA
35
36     reg p[7:0][7:0]; // double array for partial products
37     integer i,j;
38
39     always@(a or b)
40     begin
41         for(i=0;i<=5;i=i+1) // nested for loops.
42             for(j=0;j<=5;j=j+1)
43                 p[i][j]<= a[j] & b[i]; // to generate partial products.
44     end
45
46 endmodule

```

```

47
48 Halfadder HA0 (p[1][0],p[0][1],s1,c1);
49 Fulladder FA0 (p[0][2],p[1][1],p[2][0],s2,c2);
50 Fulladder FA1 (p[0][3],p[1][2],p[2][1],s3,c3);
51 Fulladder FA2 (p[0][4],p[1][3],p[2][2],s4,c4);
52 Fulladder FA3 (p[0][5],p[1][4],p[2][3],s5,c5);
53 Halfadder HA1 (p[1][5],p[2][4],s6,c6);
54
55 Halfadder HA2 (p[3][1],p[4][0],s7,c7);
56 Fulladder FA4 (p[3][2],p[4][1],p[5][0],s8,c8);
57 Fulladder FA5 (p[3][3],p[4][2],p[5][1],s9,c9);
58 Fulladder FA6 (p[3][4],p[4][3],p[5][2],s10,c10);
59 Fulladder FA7 (p[3][5],p[4][4],p[5][3],s11,c11);
60 Halfadder HA3 (p[4][5],p[5][4],s12,c12);
61
62 Halfadder HA4 (s2,c1,s13,c13);
63 Fulladder FA8 (p[3][0],s3,c2,s14,c14);
64 Fulladder FA9 (s4,c3,s7,s15,c15);
65 Fulladder FA10 (s5,c4,s8,s16,c16);
66 Fulladder FA11 (s6,c5,s9,s17,c17);
67 Fulladder FA12 (p[2][5],c6,s10,s18,c18);
68
69 Halfadder HA5 (s14,c13,s19,c19);
70 Halfadder HA6 (s15,c14,s20,c20);
71 Fulladder FA13 (s16,c15,c7,s21,c21);
72 Fulladder FA14 (s17,c16,c8,s22,c22);
73 Fulladder FA15 (s18,c17,c9,s23,c23);
74 Fulladder FA16 (s11,c18,c10,s24,c24);
75 Halfadder HA7 (s12,c11,s25,c25);
76 Halfadder HA8 (p[5][5],c12,s26,c26);
77
78 Halfadder HA9 (s20,c19,s27,c27);
79 Fulladder FA17 (s21,c20,c27,s28,c28);
80 Fulladder FA18 (s22,c21,c28,s29,c29);
81 Fulladder FA19 (s23,c22,c29,s30,c30);
82 Fulladder FA20 (s24,c23,c30,s31,c31);
83 Fulladder FA21 (s25,c24,c31,s32,c32);
84 Fulladder FA22 (s26,c25,c32,s33,c33);
85 Halfadder HA10 (c26,c33,s34,c34);
86
87 assign product[0]=p[0][0];
88 assign product[1]=s1;
89 assign product[2]=s13;
90 assign product[3]=s19;
91 assign product[4]=s27;
92 assign product[5]=s28;
93 assign product[6]=s29;
94 assign product[7]=s30;
95 assign product[8]=s31;
96 assign product[9]=s32;
97 assign product[10]=s33;
98 assign product[11]=s34;
99 assign product[12]=c34;
100
101 endmodule

```

### Verilog test fixture code:

```

26 module WallaceMulTF;
27     // Inputs
28     reg [7:0] a;
29     reg [7:0] b;
30     // Outputs
31     wire [12:0] product;
32     // Instantiate the Unit Under Test (UUT)
33     WallaceMul uut (
34         .a(a),
35         .b(b),
36         .product(product)
37     );
38     initial begin
39         // Initialize Inputs
40         a = 0;
41         b = 0;
42         // Wait 100 ns for global reset to finish
43         #100;
44         // Add stimulus here
45         a=6'b110101;
46         b=6'b011011;
47     end
48 endmodule

```

### WAVEFORM:

		1,000,				
Name	Value	1999,995 ps	1999,996 ps	1999,997 ps	1999,998 ps	1999,999 ps
product[12:0]	1431			1431		
a[5:0]	53			53		
b[5:0]	27			27		

## HOME ASSIGNMENT

### TASK:

To Develop, Implement and Simulate 8x8 Dadda Wallace Tree.

### Verilog Module code:

```

23 module WallaceMul(
24     input [7:0] a,
25     input [7:0] b,
26     output [16:0] product
27 );
28
29     wire
30     s1,s2,s3,s4,s5,s6,s7,s8,s9,s10,s11,s12,s13,s14,s15,s16,s17,s18,s19,s20,s21,
31     s22,s23,s24,s25,s26,s27,s28,s29,s30,s31,s32,s33,s34,s35,s36,s37,s38,s39,s40,s41,
32     s42,s43,s44,s45,s46,s47,s48,s49,s50,s51,s52,s53,s54,s55,s56,s57,s58,s59,s60,s61,
33     s62,s63,s64,c1,c2,c3,c4,c5,c6,c7,c8,c9,c10,c11,c12,c13,c14,c15,c16,c17,c18,c19,c20,c21,
34     c22,c23,c24,c25,c26,c27,c28,c29,c30,c31,c32,c33,c34,c35,c36,c37,c38,c39,c40,c41,
35     c42,c43,c44,c45,c46,c47,c48,c49,c50,c51,c52,c53,c54,c55,c56,c57,c58,c59,c60,c61,c62,c63,c6
36     // sums & carries generated by FA
37
38     reg p[7:0][7:0]; // double array for partial products
39     integer i,j;
40
41
42     always@(a or b)
43     begin
44         for(i=0;i<=8;i=i+1) // nested for loops.
45             for(j=0;j<=8;j=j+1)
46                 p[i][j]<= a[j] & b[i]; // to generate partial products.
47
48     end
49     Halfadder HA0 (p[0][1],p[1][0],s1,c1);
50     Fulladder FA0 (p[0][2],p[1][1],p[2][0],s2,c2);
51     Fulladder FA1 (p[0][3],p[1][2],p[2][1],s3,c3);
52     Fulladder FA2 (p[0][4],p[1][3],p[2][2],s4,c4);
53     Fulladder FA3 (p[0][5],p[1][4],p[2][3],s5,c5);
54     Fulladder FA4 (p[0][6],p[1][5],p[2][4],s6,c6);
55     Fulladder FA5 (p[0][7],p[1][6],p[2][5],s7,c7);
56     Halfadder HA1 (p[1][7],p[2][6],s8,c8);
57
58     Halfadder HA2 (p[3][1],p[4][0],s9,c9);
59     Fulladder FA6 (p[3][2],p[4][1],p[5][0],s10,c10);
60     Fulladder FA7 (p[3][3],p[4][2],p[5][1],s11,c11);
61     Fulladder FA8 (p[3][4],p[4][3],p[5][2],s12,c12);
62     Fulladder FA9 (p[3][5],p[4][4],p[5][3],s13,c13);
63     Fulladder FA10 (p[3][6],p[4][5],p[5][4],s14,c14);
64     Fulladder FA11 (p[3][7],p[4][6],p[5][5],s15,c15);
65     Halfadder HA3 (p[4][7],p[5][6],s16,c16);
66
67     Halfadder HA4 (s2,c1,s17,c17);
68     Fulladder FA12 (p[3][0],s3,c2,s18,c18);
69     Fulladder FA13 (s4,c3,s9,s19,c19);
70     Fulladder FA14 (s5,c4,s10,s20,c20);
71     Fulladder FA15 (s6,c5,s11,s21,c21);
72     Fulladder FA16 (s7,c6,s12,s22,c22);
73     Fulladder FA18 (s8,c7,s13,s23,c23);
74     Fulladder FA19 (p[2][7],c8,s14,s24,c24);
75

```

```

76 Halfadder HA5 (p[6][0],c10,s25,c25);
77 Fulladder FA20 (p[6][1],p[7][0],c11,s26,c26);
78 Fulladder FA21 (p[6][2],p[7][1],c12,s27,c27);
79 Fulladder FA22 (p[6][3],p[7][2],c13,s28,c28);
80 Fulladder FA23 (p[6][4],p[7][3],c14,s29,c29);
81 Fulladder FA24 (p[6][5],p[7][4],c15,s30,c30);
82 Fulladder FA25 (p[6][6],p[7][5],c16,s31,c31);
83 Halfadder HA6 (p[6][7],p[7][6],s32,c32);
84
85 Halfadder HA7 (s18,c17,s33,c33);
86 Halfadder HA8 (s19,c18,s34,c34);
87 Fulladder FA26 (s20,c19,c9,s35,c35);
88 Fulladder FA27 (s21,c20,s25,s36,c36);
89 Fulladder FA28 (s22,c21,s26,s37,c37);
90 Fulladder FA29 (s23,c22,s27,s38,c38);
91 Fulladder FA30 (s24,c23,s28,s39,c39);
92 Fulladder FA31 (s15,c24,s29,s40,c40);
93 Halfadder HA9 (s16,s30,s41,c41);
94 Halfadder HA10 (p[5][7],s31,s42,c42);
95
96 Halfadder HA11 (s34,c33,s43,c43);
97 Halfadder HA12 (s35,c34,s44,c44);
98 Halfadder HA13 (s36,c35,s45,c45);
99 Fulladder FA32 (s37,c36,c25,s46,c46);
100 Fulladder FA33 (s38,c37,c26,s47,c47);
101 Fulladder FA34 (s39,c38,c27,s48,c48);
102 Fulladder FA35 (s40,c39,c28,s49,c49);
103 Fulladder FA36 (s41,c40,c29,s50,c50);
104 Fulladder FA37 (s42,c41,c30,s51,c51);
105 Fulladder FA38 (s32,c42,c31,s52,c52);
106 Halfadder HA14 (p[7][7],c32,s53,c53);
107
108 Halfadder HA15 (s44,c43,s54,c54);
109 Fulladder FA39 (s45,c44,c54,s55,c55);
110 Fulladder FA40 (s46,c45,c55,s56,c56);
111 Fulladder FA41 (s47,c46,c56,s57,c57);
112 Fulladder FA42 (s48,c47,c57,s58,c58);
113 Fulladder FA43 (s49,c48,c58,s59,c59);
114 Fulladder FA44 (s50,c49,c59,s60,c60);
115 Fulladder FA45 (s51,c50,c60,s61,c61);
116 Fulladder FA46 (s52,c51,c61,s62,c62);
117 Fulladder FA47 (s53,c52,c62,s63,c63);
118 Halfadder HA16 (c53,c63,s64,c64);
119
120
121 assign product[0]=p[0][0];
122 assign product[1]=s1;
123 assign product[2]=s17;
124 assign product[3]=s33;
125 assign product[4]=s43;
126 assign product[5]=s54;
127 assign product[6]=s55;
128 assign product[7]=s56;
129 assign product[8]=s57;
130 assign product[9]=s58;
131 assign product[10]=s59;
132 assign product[11]=s60;
133 assign product[12]=s61;
134 assign product[13]=s62;
135 assign product[14]=s63;
136 assign product[15]=s64;
137 assign product[16]=c64;
138
139
140 endmodule
141



```

### Verilog test fixture code:

```

26 module WallaceMulTF;
27
28 // Inputs
29 reg [7:0] a;
30 reg [7:0] b;
31 // Outputs
32 wire [16:0] product;
33 // Instantiate the Unit Under Test (UUT)
34 WallaceMul uut (
35     .a(a),
36     .b(b),
37     .product(product)
38 );
39 initial begin
40     // Initialize Inputs
41     a = 0;
42     b = 0;
43     // Wait 100 ns for global reset to finish
44     #100;
45     // Add stimulus here
46     a=8'b01101011;
47     b=8'b11111010;
48
49 end
50 endmodule

```

  **WAVEFORM:****Schematic Diagram:****CONCLUSION:**

In this lab, We have developed 4x4 and 6x6 wallace tree in our lab task. Developing 4x4 wallace tree takes 4 bit values as input and generates 8 bits output. Similarly developing 6x6 wallace tree takes 6 bit values as input and generates 12 bits output. We Developed 8x8 wallace tree in our home assignment which takes 8 bit values as input and generates 16 bits output.

So in general we learn how to multiply integers as binary bits using Dadda Wallace Tree. Using the ISE Design Suite, we also utilized data flow modelling to simulate multiplying. We also produced a wave output in which we can see the characteristics of the output after performing multiplication.