


LAB 14 OPEN ENDED LAB

OBJECTIVE:

To design, implement and simulate different finite state diagrams (Combinations) using mealy machine concept.


HARDWARE / SOFTWARE REQUIRED:

 HARDWARE: The mealy state machine block diagram consists of two parts namely [combinational logic](#) as well as memory. The memory in the machine can be used to provide some of the previous outputs as combinational logic inputs.



Mealy State Machine Block Diagram

SOFTWARE: We have used a software Xilinx 14.7 for performing this task.

 DIAGRAM 01:

State Diagram of Mealy State Machine

METHODOLOGY:

Based on the current inputs as well as states, this machine can produce outputs. Thus, the outputs can be suitable only at positive otherwise negative of the CLK signal.

The above state diagram of mealy state machine mainly includes three states namely A, B, and C. These three states are tagged within the circles as well as every circle communicates with one state. Conversions

among these three states are signified by directed lines. In the above diagram, the inputs and outputs are denoted with 0/0, 1/0, and 1/1. Based on the input value, there are two conversions from every state.

How can we choose between Mealy state machine & Moore state machine :

Generally, the amount of required states in the mealy machine is below or equivalent to the number of required states in Moore state machine. There is an equal Moore state machine for every Mealy state machine. As a result, based on the necessity we can employ one of them.

SOURCE CODE:

Verilog Module Code:

```

2 //Umer(CE-118-2020)
3 module VendingMealyMachine (open, Clk, Reset, b);
4     output open;
5     input Clk;
6     input Reset;
7     input b;
8
9     reg open, next_open;
10    reg [1:0] state;
11    reg [1:0] next_state;
12
13    parameter [1:0] A = 2'b00;
14    parameter [1:0] B = 2'b01;
15    parameter [1:0] C = 2'b10;
16
17    always@(b or state)
18    begin
19        case(state)
20
21            A:begin
22                if(b) begin
23                    next_state=B;
24                    next_open=0;
25                end
26                else begin
27                    next_state=A;
28                    next_open=0;
29                end
30            end
31
32            B:begin
33                if(b) begin
34                    next_state=B;
35                    next_open=0;
36                end
37                else begin
38                    next_state=C;
39                    next_open=0;
40                end
41            end
42
43            C:begin
44                if(b) begin
45                    next_state=B;
46                    next_open=1;
47                end
48                else begin
49                    next_state=0;
50                    next_open=0;
51                end
52            end
53        endcase
54    end
55 end

```

```

58     always @(posedge Clk)
59     begin
60         if(Reset )           ///|| (!N && !D)) s
61         begin
62             state <= A;
63             open<=0;
64         end
65
66         else begin
67             state<=next_state;
68             open<=next_open;
69         end
70     end
71 endmodule

```

Verilog Test Fixture Code:



```

1  module SD_tf;
2
3      // Inputs
4      reg Clk;
5      reg Reset;
6      reg b;
7
8      // Outputs
9      wire open;
10
11     // Instantiate the Unit Under Test (UUT)
12     VendingMealyMachine uut (
13         .open(open),
14         .Clk(Clk),
15         .Reset(Reset),
16         .b(b)
17     );
18
19     parameter PERIOD=100;
20
21     always
22     begin
23
24         Clk=1;
25         #(PERIOD/2);
26
27         Clk=0;
28         #(PERIOD/2);

```

```
29     end
30
31     initial begin
32         // Initialize Inputs
33
34         Reset = 1;
35         b = 0;
36
37         // Wait 100 ns for global reset to finish
38         // Add stimulus here
39
40         #100;
41
42         Reset = 0;
43         b = 1;
44         #100;
45
46
47         b = 1;
48         #100;
49
50
51         b = 1;
52         #100;
53
54         b = 0;
55         #100;
56
57
58         b = 1;
59         #100;
60
61         b = 1;
62         #100;
63
64         b = 0;
65         #100;
66
67         b = 1;
68         #100;
69
70         b = 1;
71         #100;
72
73     end
74
75 endmodule
```

Result / Wave Form:

  **DIAGRAM 02:****METHODOLOGY:**

Based on the current inputs as well as states, this machine can produce outputs. Thus, the outputs can be suitable only at positive otherwise negative of the CLK signal.

The above state diagram of mealy state machine mainly includes three states namely S0, S1, and S2.

These three states are tagged within the circles as well as every circle communicates with one state.

Conversions among these three states are signified by directed lines. In the above diagram, the inputs and outputs are denoted with 0/0, 0/1, 1/0, and 1/1. Based on the input value, there are two conversions from every state.

SOURCE CODE:

Verilog Module Code:

```

2  //Umer(CE-118-2020)
3  module VendingMealyMachine(open, Clk, Reset, b);
4      output open;
5      input Clk;
6      input Reset;
7      input b;
8
9      reg open, next_open;
10     reg [1:0] state;
11     reg [1:0] next_state;
12
13     parameter [1:0] s0 = 2'b00;
14     parameter [1:0] s1 = 2'b01;
15     parameter [1:0] s2 = 2'b10;
16
17
18     always@(b or state)
19     begin

```

```
20     case(state)
21
22         s0:begin
23             if(b) begin
24                 next_state=s1;
25                 next_open=0;
26             end
27             else begin
28                 next_state=s2;
29                 next_open=0;
30             end
31
32         end
33
34         s1:begin
35             if(b) begin
36                 next_state=s1;
37                 next_open=1;
38             end
39             else begin
40                 next_state=s2;
41                 next_open=1;
42             end
43
44         end
45
46         s2:begin
47             if(b) begin
48                 next_state=s1;
49                 next_open=0;
50             end
51             else begin
52                 next_state=s2;
53                 next_open=0;
54             end
55         end
56     endcase
57 end
58
59 always @(posedge Clk)
60 begin
61     if(Reset )          //|| (!N && !D)) s
62     begin
63         state <=s0;
64         open<=0;
65     end
66
67     else begin
68         state<=next_state;
69         open<=next_open;
70     end
71 end
72 endmodule
```

Verilog Test Fixture Code:


```
1  module SD_tf;
2
3      // Inputs
4      reg Clk;
5      reg Reset;
6      reg b;
7
8      // Outputs
9      wire open;
10
11     // Instantiate the Unit Under Test (UUT)
12     VendingMealyMachine uut (
13         .open(open),
14         .Clk(Clk),
15         .Reset(Reset),
16         .b(b)
17     );
18
19     parameter PERIOD=100;
20
21     always
22     begin
23
24         Clk=1;
25         #(PERIOD/2);
26
27         Clk=0;
28         #(PERIOD/2);
29     end
30
31     initial begin
32         // Initialize Inputs
33
34         Reset = 1;
35         b = 0;
36
37         // Wait 100 ns for global reset to finish
38         // Add stimulus here
39
40         #100;
41
42         Reset = 0;
43         b = 1;
44         #100;
45
46         b = 1;
47         #100;
```

```

49      b = 1;
50      #100;
51
52      b = 0;
53      #100;
54
55
56      b = 1;
57      #100;
58
59      b = 1;
60      #100;
61
62      b = 0;
63      #100;
64
65      b = 1;
66      #100;
67
68      b = 0;
69      #100;
70
71      end
72
73      endmodule

```

Result / Wave Form:

 

CONCLUSION:

From this open ended lab we learned how to design, implement and simulate different finite state diagrams (combinations) using mealy machine concept.

Using the ISE Design Suite, We also produced a wave output in which we can see the characteristics of the output after performing these tasks.

Implementing a Mealy machine can be a useful tool in designing and implementing a finite state machine for a specific application. It allows for the output of the machine to be dependent on both the current input and current state, which can be beneficial in certain situations where the output needs to be generated in real-time based on the current input. However, it is important to carefully consider the specific requirements and constraints of the application before deciding whether a Mealy machine is the appropriate solution. It may be necessary to evaluate the trade-offs and limitations of using a Mealy machine, such as the potential for increased complexity in the design and implementation, compared to other types of finite state machines. Overall, the decision to use a Mealy machine should be based on a thorough analysis of the specific needs of the application and the resources available for implementation.