

LAB 09

OBJECTIVE

Develop, implement and Simulate Moore Machine using behavioral modeling

Lab Task 1

Implement and simulate Vending Moore Machine

Verilog Module Code:

```
21 module VendingMooreMachine (open, Clk, Reset, N, D);
22     output open;
23     input Clk;
24     input Reset;
25     input N;
26     input D;
27
28     reg open;
29     reg [1:0] state;
30     reg [1:0] next_state;
31
32     parameter [1:0] zero = 2'b00;
33     parameter [1:0] five = 2'b01;
34     parameter [1:0] ten = 2'b10;
35     parameter [1:0] fifteen = 2'b11;
36
37     always@ (N or D or state) // Next State determination
38     begin
39         case (state)
40
41             zero: begin
42                 if (N) begin
43                     next_state = five;
44                 end
45                 else if (D) begin
46                     next_state = ten;
47                 end
48                 else begin
49                     next_state = zero;
50                 end
51             end
52
53             five: begin
54                 if (N) begin
55                     next_state = ten;
56                 end
57                 else if (D) begin
58                     next_state = fifteen;
59                 end
60                 else begin
61                     next_state = five;
62                 end
63             end
64         end case
65     end
```

```
65         ten:begin
66             if (N) begin
67                 next_state=fifteen;
68             end
69             else if (D) begin
70                 next_state=fifteen;
71             end
72             else begin
73                 next_state=ten;
74             end
75         end
76
77         fifteen:begin
78
79             if (N) begin
80                 next_state=five;
81             end
82             else if (D) begin
83                 next_state=ten;
84             end
85             else begin
86                 next_state=0;
87             end
88         end
89     endcase
90 end
91
94 always @(posedge Clk) // State Registers
95 begin
96
97     if (Reset )
98     begin
99         state <= zero;
100     end
101
102     else begin
103         state<=next_state;
104     end
105 end
106
107 always@(state) // Output determination
108 begin
109     case (state)
110
111         zero:begin
112             open<=0;
113         end
114
115         five:begin
116             open<=0;
117         end
118
119         ten:begin
120             open<=0;
121         end
```


```
123             fifteen:begin
124                 open<=1;
125             end
126
127         endcase
128     end
129 endmodule
```

Verilog Test Fixture Code:

```
24 module VMMoTF;
25
26     // Inputs
27     reg Clk;
28     reg Reset;
29     reg N;
30     reg D;
31
32     // Outputs
33     wire open;
34
35     // Instantiate the Unit Under Test (UUT)
36     VendingMooreMachine uut (
37         .open(open),
38         .Clk(Clk),
39         .Reset(Reset), |
40         .N(N),
41         .D(D)
42     );
43
44     parameter PERIOD=100;
45
46     always
47     begin
48
49         Clk=1;
50         #(PERIOD/2);
```

```
52     Clk=0;
53     #(PERIOD/2);
54 end
55
56
57 initial begin
58     // Initialize Inputs
59
60     Reset = 1;
61     N = 0;
62     D = 0;
63
64     // Wait 100 ns for global reset to finish
65
66
67     // Add stimulus here
68
69     // Case: 3 Nikles are inserted
70     #100; N=0;D=0;Reset=0;
71
72     #100; N=1;D=0;
73     #100; N=1;D=0;
74     #100; N=1;D=0;
75
76 //#100;  N=0;D=0;Reset=0;
77
78 // Case: 1 Nikel 1 Dime are inserted
79 //#100;  N=0;D=0;
80     #100; N=1;D=0;
81     #100; N=0;D=1;
82
83 //#100;  N=0;D=0;Reset=0;
84 // Case: 2 Dimes are inserted
85 //#100;  N=0;D=0;
86
87     #100; N=0;D=1;
88     #100; N=0;D=1;
89     #100; N=0;D=0;
90
91
92 end
93
94
95 endmodule
```

WAVEFORM:

 

Lab Task 2

To develop a sequence detector

Sequence: 1101

Verilog Module Code:

```

21 module SequenceMooreFSM(Clk,Reset,sequence_in,detector_out);
22     input Clk;
23     input Reset;
24     input sequence_in;
25     output detector_out;
26
27
28     reg detector_out;
29     reg [2:0]state;
30     reg [2:0]next_state;
31
32
33     parameter [2:0]S0 = 3'b000;
34     parameter [2:0]S1 = 3'b001;
35     parameter [2:0]S2 = 3'b010;
36     parameter [2:0]S3 = 3'b011;
37     parameter [2:0]S4 = 3'b100;
38
39
40     always@(sequence_in or state) // Next State determination
41     begin
42         case(state)
43

```

```
44         S0:begin
45             if(sequence_in) begin
46                 next_state=S1;
47             end
48
49             else begin
50                 next_state=S0;
51             end
52         end
53
54         S1:begin
55             if(sequence_in) begin
56                 next_state=S2;
57             end
58
59             else begin
60                 next_state=S0;
61             end
62         end
63
64         S2:begin
65             if(sequence_in) begin
66                 next_state=S2;
67             end
68
69             else begin
70                 next_state=S3;
71             end
72         end
73
74         S3:begin
75
76             if(sequence_in) begin
77                 next_state=S4;
78             end
79
80             else begin
81                 next_state=S0;
82             end
83         end
84
85         S4:begin
86
87             if(sequence_in) begin
88                 next_state=S1;
89             end
90
91             else begin
92                 next_state=S0;
93             end
94         end
95
96     endcase
97 end
--
```

```

100     always @(posedge Clk) // State Registers
101     begin
102         if (Reset)
103             begin
104                 state <= S0;
105             end
106         else begin
107             state <= next_state;
108         end
109     end
110
111     always@(state) // output determination
112     begin
113         case (state)
114             S0:begin
115                 detector_out <= 0;
116             end
117             S1:begin
118                 detector_out <= 0;
119             end
120             S2:begin
121                 detector_out <= 0;
122             end
123             S3:begin
124                 detector_out <= 0;
125             end
126             S4:begin
127                 detector_out <= 1;
128             end
129         endcase
130     end
131
132     endcase
133 end
134
135 endmodule
136
137
138
139
140
141

```

Verilog Test Fixture Code:

```


24 module SMFSMIF;
25     // Inputs
26     reg Clk;
27     reg Reset;
28     reg sequence_in;
29     // Outputs
30     wire detector_out;
31     // Instantiate the Unit Under Test (UUT)
32     SequenceModelFSM uut (
33         .Clk(Clk),
34         .Reset(Reset),
35         .sequence_in(sequence_in),
36         .detector_out(detector_out)
37     );
38
39     parameter PERIOD=100;
40
41     always
42     begin
43         Clk=1;
44         #(PERIOD/2);
45     end
46
47
48
49

```

```

50     Clk=0;
51     #(PERIOD/2);
52 end
53 initial begin
54     // Initialize Inputs
55
56     Reset = 1;
57     sequence_in = 0;
58     // Wait 100 ns for global reset to finish
59     // Add stimulus here
60     #100; Reset=0;
61     #100; sequence_in = 1;
62     #100; sequence_in = 1;
63     #100; sequence_in = 0;
64     #100; sequence_in = 1;
65     #100; sequence_in = 0;
66     #100; sequence_in = 0;
67     #100; sequence_in = 0;
68     #100; sequence_in = 1;
69     #100; sequence_in = 0;
70     #100; sequence_in = 1;
71     #100; sequence_in = 0;
72     #100; sequence_in = 0;
73     #100; sequence_in = 1;
74 end
75 endmodule

```

 WAVEFORM:**CONCLUSION:**

In this lab, we learned how to develop Vending Machine and also develop sequence detector using Moore machine. Using the ISE Design Suite, We also produced a wave output in which we can see the characteristics of the output after performing these task.

We also learned about the Moore machine concept in this lab and carried out activities involving this state machine. We do two tasks. The first is a vending machine that was designed with a sequence detector and was able to work as planned by accepting the utilising the proper input sequence and releasing the appropriate product. And the second one, a sequence detector, proved how well Moore's machine worked at detecting particular sequences by precisely identifying the input sequence and producing the right output signal. In the end, this idea proved the adaptability and dependability of Moore's machine in the creation of useful systems.