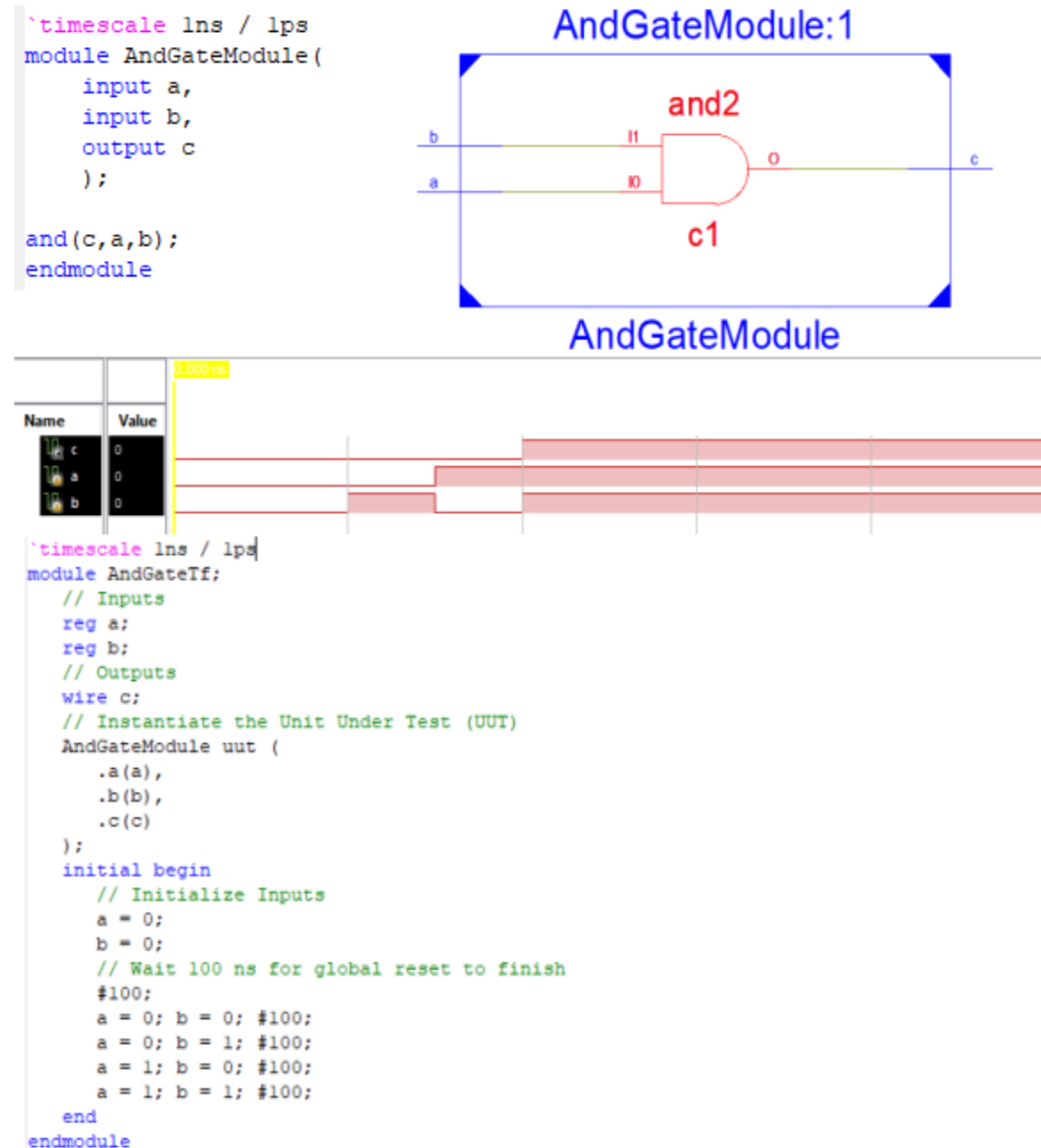


LAB#01

Introduction to Verilog Language, Gate Level Modelling and Example.

OBJECTIVE: Introduction to Verilog Language, Gate Level Modelling and Example

Lab Tasks: • Develop and implement different logic gates (AND, OR, NOT, XOR) using Gate Level Modeling in Verilog.



1. To Develop, Implement and Simulate AND gate using Verilog Gate Level Modelling.

2. To Develop, Implement and Simulate OR gate using Verilog Gate Level Modelling.

```

`timescale 1ns / 1ps
module OrGateModule(
    input a,
    input b,
    output c
);
    or(c,a,b);
endmodule

```

 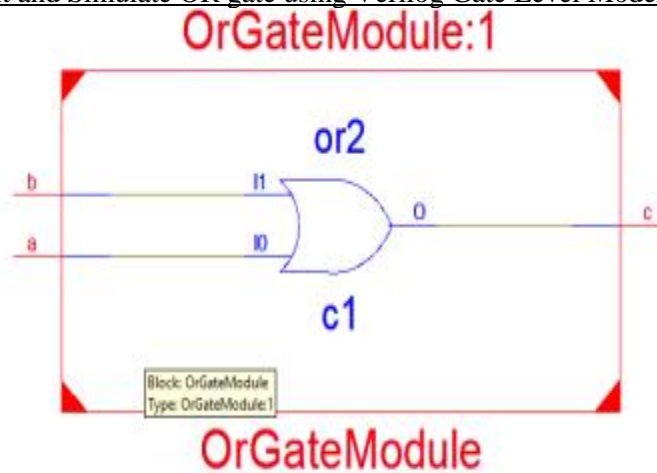

```

`timescale 1ns / 1ps
module OrGateTf;
    // Inputs
    reg a;
    reg b;
    // Outputs
    wire c;
    // Instantiate the Unit Under Test (UUT)
    OrGateModule uut (
        .a(a),
        .b(b),
        .c(c)
    );
    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;
        // Wait 100 ns for global reset to finish
        #100;
        a = 0; b = 0; #100;
        a = 0; b = 1; #100;
        a = 1; b = 0; #100;
        a = 1; b = 1; #100;
        // Add stimulus here
    end
endmodule

```


3. To Develop, Implement and Simulate XOR gate using Verilog Gate Level Modelling

```

`timescale 1ns / 1ps
module XorGateModule(
    input a,
    input b,
    output c
);

xor(c,a,b);
endmodule

```

 

```

`timescale 1ns / 1ps
module XorGateTf;
    // Inputs
    reg a;
    reg b;
    // Outputs
    wire c;
    // Instantiate the Unit Under Test (UUT)
    XorGateModule uut (
        .a(a),
        .b(b),
        .c(c)
    );
    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;
        // Wait 100 ns for global reset to finish
        #100;
        a = 0; b = 0; #100;
        a = 0; b = 1; #100;
        a = 1; b = 0; #100;
        a = 1; b = 1; #100;
        // Add stimulus here
    end
end
endmodule


```

4. To Develop, Implement and Simulate NOT gate using Verilog Gate Level Modelling

```

`timescale 1ns / 1ps
module NotGateModule(
    input a,
    output b
);
    not(b,a);
endmodule

```

 

```

`timescale 1ns / 1ps
module NotGateTf;
    // Inputs
    reg a;
    // Outputs
    wire b;
    // Instantiate the Unit Under Test (UUT)
    NotGateModule uut (
        .a(a),
        .b(b)
    );
    initial begin
        // Initialize Inputs
        a = 0;

        // Wait 100 ns for global reset to finish
        #100;
        a=0; #100;
        a=1; #100;

        // Add stimulus here
    end
endmodule

```